

Pr. 2 a) - pokračování

Pro jednoduchý výpočet nahradíme impedance admitancemi

$$\bar{Y}_U = \frac{1}{\bar{Z}_U} \quad , \quad \bar{Y}_V = \frac{1}{\bar{Z}_V} \quad , \quad \bar{Y}_W = \frac{1}{\bar{Z}_W} \quad , \quad \bar{Y}_N = \frac{1}{\bar{Z}_N}$$

či obdobně do rovnice 1. Kirchhoffova zákona pro uzel  $Q_2$ :

$$\begin{aligned} & -\bar{Y}_U (\bar{U}_{OU} - \bar{U}_N) - \bar{Y}_W (\bar{U}_{OW} - \bar{U}_N) + \bar{Y}_N \bar{U}_N = 0 \\ & -\bar{Y}_U \bar{U}_{OU} + \bar{Y}_U \bar{U}_N - \bar{Y}_V \bar{U}_{OV} + \bar{Y}_V \bar{U}_N - \bar{Y}_W \bar{U}_{OW} + \bar{Y}_W \bar{U}_N + \bar{Y}_N \bar{U}_N = 0 \\ & \bar{U}_N (\bar{Y}_U + \bar{Y}_V + \bar{Y}_W + \bar{Y}_N) = \bar{Y}_U \bar{U}_{OU} + \bar{Y}_V \bar{U}_{OV} + \bar{Y}_W \bar{U}_{OW} \\ & \bar{U}_N = \frac{\bar{Y}_U \bar{U}_{OU} + \bar{Y}_V \bar{U}_{OV} + \bar{Y}_W \bar{U}_{OW}}{\bar{Y}_U + \bar{Y}_V + \bar{Y}_W + \bar{Y}_N} \end{aligned}$$

Hledané proudy:

$$\bar{I}_U = \frac{\bar{U}_U}{\bar{Z}_U} = \frac{\bar{U}_{OU} - \bar{U}_N}{\bar{Z}_U}$$

$$\bar{I}_V = \frac{\bar{U}_V}{\bar{Z}_V} = \frac{\bar{U}_{OV} - \bar{U}_N}{\bar{Z}_V}$$

$$\bar{I}_W = \frac{\bar{U}_W}{\bar{Z}_W} = \frac{\bar{U}_{OW} - \bar{U}_N}{\bar{Z}_W}$$

$$\bar{I}_N = \frac{\bar{U}_N}{\bar{Z}_N} \quad \text{nebo} \quad \bar{I}_N = \bar{I}_U + \bar{I}_V + \bar{I}_W$$

b)  $\bar{Z}_U, \bar{Z}_V, \bar{Z}_W, \bar{Z}_U \neq \bar{Z}_V \neq \bar{Z}_W, \bar{Z}_N \rightarrow \infty \Rightarrow \bar{Y}_N = 0$

fázory napětí zdrojů  $\bar{U}_{OU}, \bar{U}_{OV}, \bar{U}_{OW}$

$$\bar{U}_N = \frac{\bar{Y}_U \bar{U}_{OU} + \bar{Y}_V \bar{U}_{OV} + \bar{Y}_W \bar{U}_{OW}}{\bar{Y}_U + \bar{Y}_V + \bar{Y}_W} \Rightarrow \bar{U}_N \text{ je reálné}$$

$\bar{U}_N >$  než s nulovým vodičem

vliv nesymetrie se projeví nejvíce.

c)  $\bar{Z}_U, \bar{Z}_W, \bar{Z}_V, \bar{Z}_U \neq \bar{Z}_V \neq \bar{Z}_W, \bar{Z}_N = 0 \Rightarrow \bar{Y}_N \rightarrow \infty$

fázory napětí zdrojů  $\bar{U}_{OU}, \bar{U}_{OV}, \bar{U}_{OW}$  (nulový vodič je dočerný)

$$\bar{U}_N = 0$$

$$\bar{I}_U = \frac{\bar{U}_{OU}}{\bar{Z}_U} \quad , \quad \bar{I}_V = \frac{\bar{U}_{OV}}{\bar{Z}_V} \quad , \quad \bar{I}_W = \frac{\bar{U}_{OW}}{\bar{Z}_W}$$

$$\bar{I}_N = \bar{I}_U + \bar{I}_V + \bar{I}_W$$