

Cvičení PJS

Přechodné děje na transformátoru

2021

ZČU, FEL, KEE, Karel Noháč

% Zakladni technicke parametry transformatoru	
Un1=110	Un1 = 110
Un2=22	Un2 = 22
Snt=10	Snt = 10
dP0p=0.3	dP0p = 0.30000
dPfep=dP0p	dPfep = 0.30000
dPkp=1	dPkp = 1
dPcup=dPkp	dPcup = 1
Ukp=10	Ukp = 10
I0p=1	I0p = 1
frekv=50	frekv = 50
omega=2*pi*frekv	omega = 314.16

% Vypocty parametru nahraneho schematu	
Znt=Un1^2/Snt	Znt = 1210
Rk=(dPkp/100)*(Un1^2/Snt)	Rk = 12.100
Rk1=Rk/2	Rk1 = 6.0500
Zk=(Ukp/100)*(Un1^2/Snt)	Zk = 121
Xs=sqrt(Zk^2-Rk^2)	Xs = 120.39
Ls=Xs/omega	Ls = 0.38322
Ls1=Ls/2	Ls1 = 0.19161
Gfe=(dP0p/100)*(Snt/Un1^2)	Gfe = 0.0000024793
Rfe=1/Gfe	Rfe = 403333.33333
Y0=(I0p/100)*(Snt/Un1^2)	Y0 = 0.0000082645
Xh=1/sqrt(Y0^2-Gfe^2)	Xh = 126842.46524
Lh=Xh/omega	Lh = 403.75

% Kontrola pres komplexni vyjadreni impedance Zk a admitance Y0

$$Zk2=abs(Rk+i*Xs)$$

$$Y02=abs(1/Rfe + 1/(i*Xh))$$

$$Zk2 = 121$$

$$Y02 = 0.0000082645$$

% Vypocet chodu naprazdno

$$\Tau0=Lh/Rk1$$

$$Z0=sqrt(Rk1^2+Xh^2)$$

$$I0m=Un1/sqrt(3)*sqrt(2)/Z0$$

$$\Psi0=atan(Xh/Rk1)$$

% Rozdíl faze oproti ryze induktivnímu proudu

$$OdchylkaPsi0=\Psi0-\pi/2$$

% Integracni konstanta

$$C0=I0m*sin(\Psi0)$$

$$\Tau0 = 66.736$$

$$Z0 = 126842.46539$$

$$I0m = 0.00070808$$

$$\Psi0 = 1.5707$$

$$OdchylkaPsi0 = -0.000047697$$

$$C0 = 0.00070808$$

% Kontrola pres komplexni vyjadreni IO

$$I0c=Un1/sqrt(3)/(Rk1+i*Xh)$$

% Amplituda alternativne

$$I0m2=sqrt(2)*abs(I0c)$$

% Faze alternativne


$$\Psi02=angle(I0c)$$

$t=[0:0.001:0.1]';$
 $I0t=C0*exp(-t/\Tau0) + I0m*sin(omega*t-\Psi0);$
 $plot(t,I0t);$

$$I0c = 0.000000023881 - 0.000500688230i$$

$$I0m2 = 0.00070808$$

$$\Psi02 = -1.5707$$

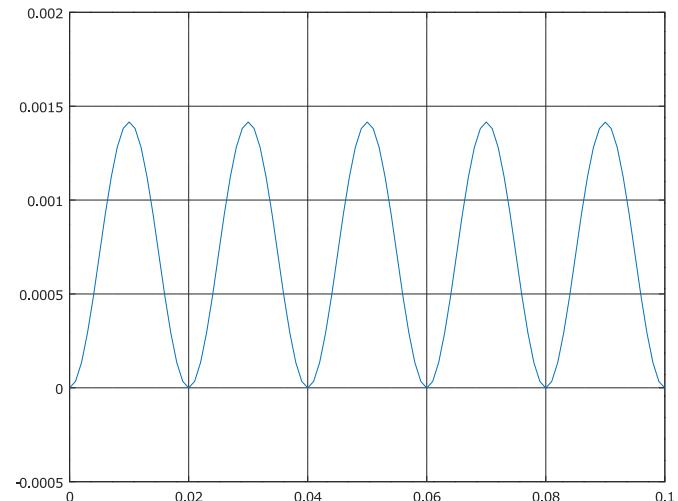

<pre>% Vypocet chodu nakratko TauK=Ls/Rk Ikm=Un1*Ukp/100/sqrt(3)*sqrt(2)/Zk PsiK=atan(Xs/Rk) % Rozdil faze oproti ryze induktivnim proudu OdchylkaPsiK=PsiK-pi/2 % Integracni konstanta Ck=Ikm*sin(PsiK)</pre>	<p>TauK = 0.031671 Ikm = 0.074227 PsiK = 1.4706 OdchylkaPsiK = -0.10017 Ck = 0.073855</p>
<pre>% Kontrola pres komplexni vyjadreni Ik Ik=Un1*Ukp/100/sqrt(3)/(Rk+i*Xs) % Amplituda alternativne Ik=abs(Ik) % Faze alternativne PsiK=angle(Ik)</pre>	<p>Ik = 0.0052486 - 0.0522233i Ik = 0.074227 PsiK = -1.4706</p>
<pre>% Kontrola pres jmenovity proud In=Snt/Un1/sqrt(3) Ikm3=In*sqrt(2) I0m3=I0p/100*In*sqrt(2) figure; Ikt=Ck*exp(-t/TauK) + Ikm*sin(omega*t-PsiK); plot(t,Ikt);</pre>	<p>In = 0.052486 Ikm3 = 0.074227 I0m3 = 0.00074227</p> 