

# Stabilita alternátoru 2022

$$Un1 = 13.5$$

$$frekv = 50$$

$$\omega = 2\pi \cdot frekv$$

% Transformatory

$$Snt1 = 200$$

$$Ukp1 = 10$$

$$Xt1 = Ukp1/100 * Un1 * Un1 / Snt1$$

$$Snt2 = 250$$

$$Ukp2 = 10$$

$$Xt2 = Ukp2/100 * Un1 * Un1 / Snt2$$

% Vedeni

$$Xv1=0.3*20/(110*110)*(Un1*Un1)$$

$$Xv=Xv1/2$$

% Nadrazena soustava

$$Xs=1.1*Un1*Un1/100$$

% Alternator

$$\cos\phi_i=0.9$$

$$Png=200$$

$$Sng=Png/\cos\phi_i$$

$$Xd=250/100 * Un1 * Un1 / Sng$$

$$Xdc=50/100 * Un1 * Un1 / Sng$$

$$Pt=150$$

$$\phi_i=\arccos(\cos\phi_i)$$

$$Qg=Pt/\cos\phi_i \cdot \sin(\phi_i)$$

$$Qg=Pt \cdot \tan(\phi_i)$$

$$Ig=(Pt-i \cdot Qg)/\sqrt{3}/Un1$$

$$Xc=Xd+Xt1+Xv+Xt2+Xs$$

$$E=i \cdot Ig \cdot Xc + Un1/\sqrt{3}$$

$$Xcc=Xdc+Xt1+Xv+Xt2+Xs$$

$$Ec=i \cdot Ig \cdot Xcc + Un1/\sqrt{3}$$

$$Us=i \cdot Ig \cdot Xs + Un1/\sqrt{3}$$

$$Ug=i \cdot Ig \cdot (Xs+Xt2+Xv+Xt1) + Un1/\sqrt{3}$$

$$\Theta=\angle(E)$$

$$\Theta_{ac}=\angle(Ec)$$

$$\text{abs}(E)$$

$$\text{abs}(Ec)$$

$$Pg=3 \cdot \text{abs}(E) \cdot Un1/\sqrt{3} / Xc \cdot \sin(\Theta)$$

$$Pg=3 \cdot \text{abs}(Ec) \cdot Un1/\sqrt{3} / Xcc \cdot \sin(\Theta_{ac})$$

$$Pmax=3 \cdot \text{abs}(E) \cdot Un1/\sqrt{3} / Xc$$

$$Pmaxc=3 \cdot \text{abs}(Ec) \cdot Un1/\sqrt{3} / Xcc$$

$$Pmax1=Pmax$$


$$Pmax2=0$$

$$Xccc=Xdc+Xt1+Xv1+Xt2+Xs$$

$$Pmax3=3 \cdot \text{abs}(Ec) \cdot Un1/\sqrt{3} / Xccc$$

$$Tm=5$$
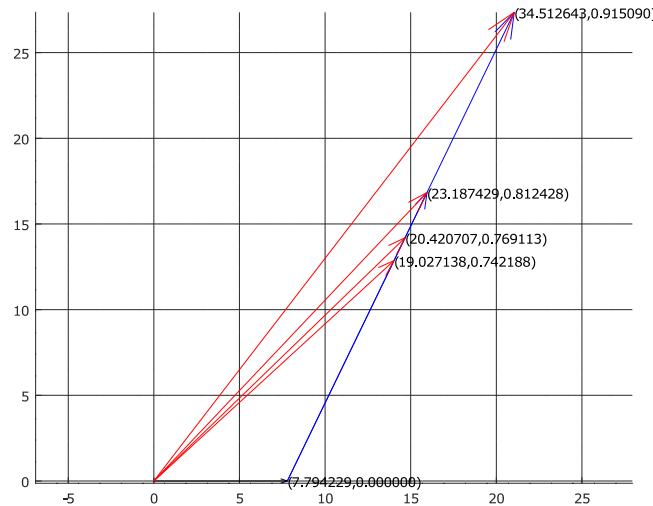
$$Jmot=Tm \cdot (Snt1 \cdot 10^6) / (\omega \cdot \omega)$$



Un1 = 13.500	Xc = 4.2643
frekv = 50	E = 21.043 + 27.355i
omega = 314.16	Xcc = 2.6240
Snt1 = 200	Ec = 15.947 + 16.833i
Ukp1 = 10	Us = 14.023 + 12.860i
Xt1 = 0.091125	Ug = 14.673 + 14.203i
Snt2 = 250	Theta = 0.91509
Ukp2 = 10	Thetac = 0.81243
Xt2 = 0.072900	ans = 34.513
Xv1 = 0.090372	ans = 23.187
Xv = 0.045186	Pg = 150.00
Xs = 2.0048	Pg = 150.00
CosFi = 0.90000	Pmax = 189.25
Png = 200	Pmaxc = 206.62
Sng = 222.22	Pmax1 = 189.25
Xd = 2.0503	Pmax2 = 0
Xdc = 0.41006	Xccc = 2.6692
Pt = 150	Pmax3 = 203.13
Fi = 0.45103	Tm = 5
Qg = 72.648	Jmot = 10132.11836
Qg = 72.648	
Ig = 6.4150 - 3.1069i	

---

% Precizni Ec

```
Iq=abs(Ig)*cos(Theta+Fi)*exp(i*angle(E))
Id=abs(Ig)*sin(Theta+Fi)*exp(i*(angle(E)-pi/2))
E=i*Id*Xc+i*Iq*Xc+Un1/sqrt(3)
Ec2=i*Id*Xcc+i*Iq*Xc+Un1/sqrt(3)
```

% Alternativne

```
Ie=Ig'*exp(i*angle(E))
Iq=real(Ie)*exp(i*angle(E))
Id=imag(Ie)*exp(i*(angle(E)-pi/2))
```

---

Iq = 0.88333 + 1.14830i	Ie = 1.4487 + 6.9790i
Id = 5.5317 - 4.2552i	Iq = 0.88333 + 1.14830i
E = 21.043 + 27.355i	Id = 5.5317 - 4.2552i
Ec2 = 14.063 + 18.282i	

---

Iq = 0.88333 + 1.14830i  
 Id = 5.5317 - 4.2552i  
 E = 21.043 + 27.355i  
 Ec2 = 14.063 + 18.282i

