
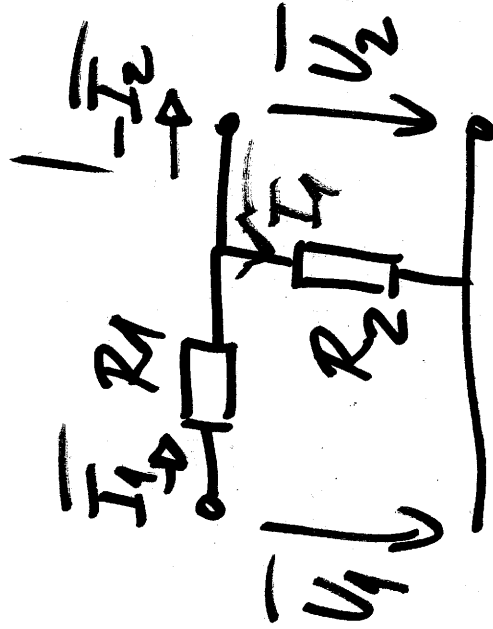


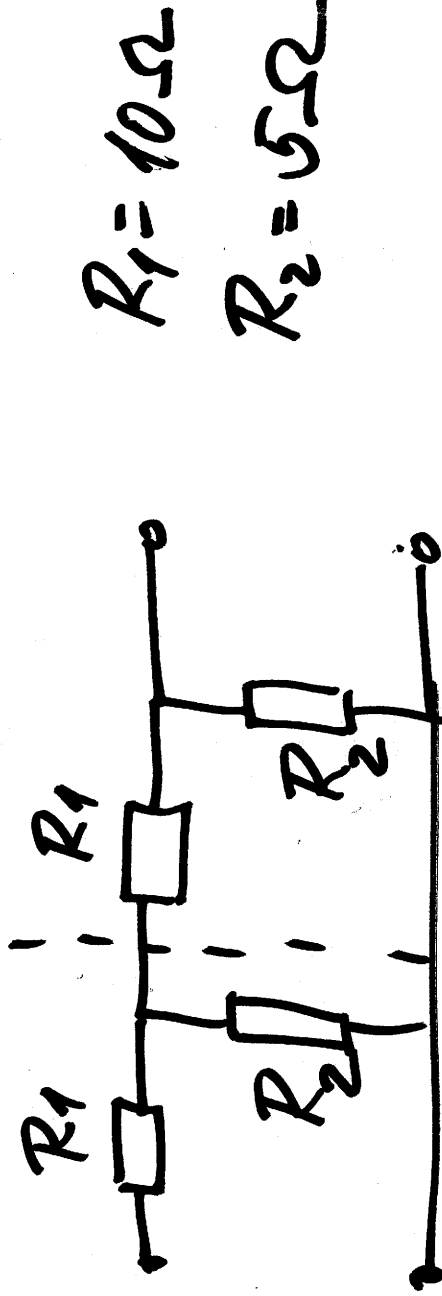
1) wähl $\bar{U}_1$ jostian $\bar{U}_2 = 60V$



$$\bar{U}_1 = \bar{a}_{11}\bar{U}_2 + \bar{a}_{12}(-\bar{I}_2)$$

$$\bar{I}_1 = \bar{a}_{21}\bar{U}_2 + \bar{a}_{22}(-\bar{I}_2)$$

$$\bar{a}_{11} = \frac{\bar{U}_1}{\bar{U}_2} \Big|_{\bar{I}_2=0} = \frac{\bar{U}_2}{R_2} \frac{(R_1 + R_2)}{\bar{U}_2} = \frac{R_1 + R_2}{R_2} = 3$$

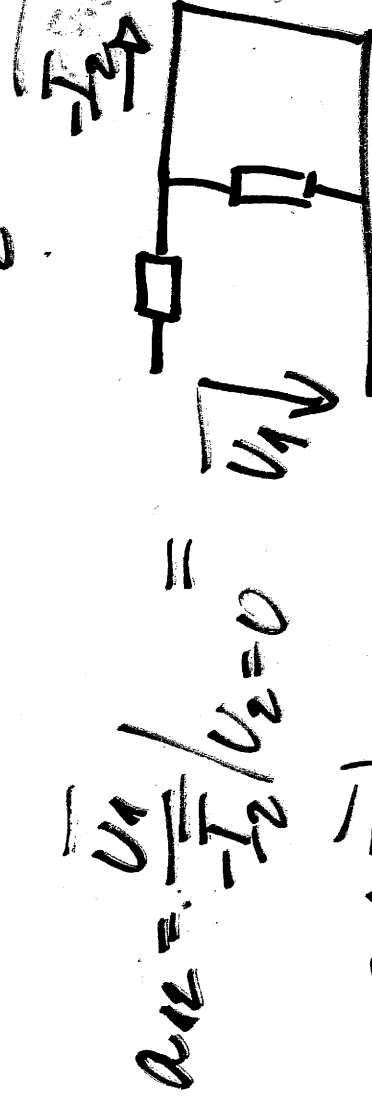

$$\bar{a}_{12} = \frac{\bar{U}_1}{-\bar{I}_2} \Big|_{\bar{U}_2=0} = \frac{R_1(-\bar{I}_2)}{-\bar{I}_2} = R_1 = 10$$